

Wednesday 12:35 - 1:40

See your exam papers in my room


PHYS A 227

→ bring a copy of the solutions!


Next Week 12th to 19th of March

No PHYS 102 Section 03 classes.

Current & Resistance & DC Circuits



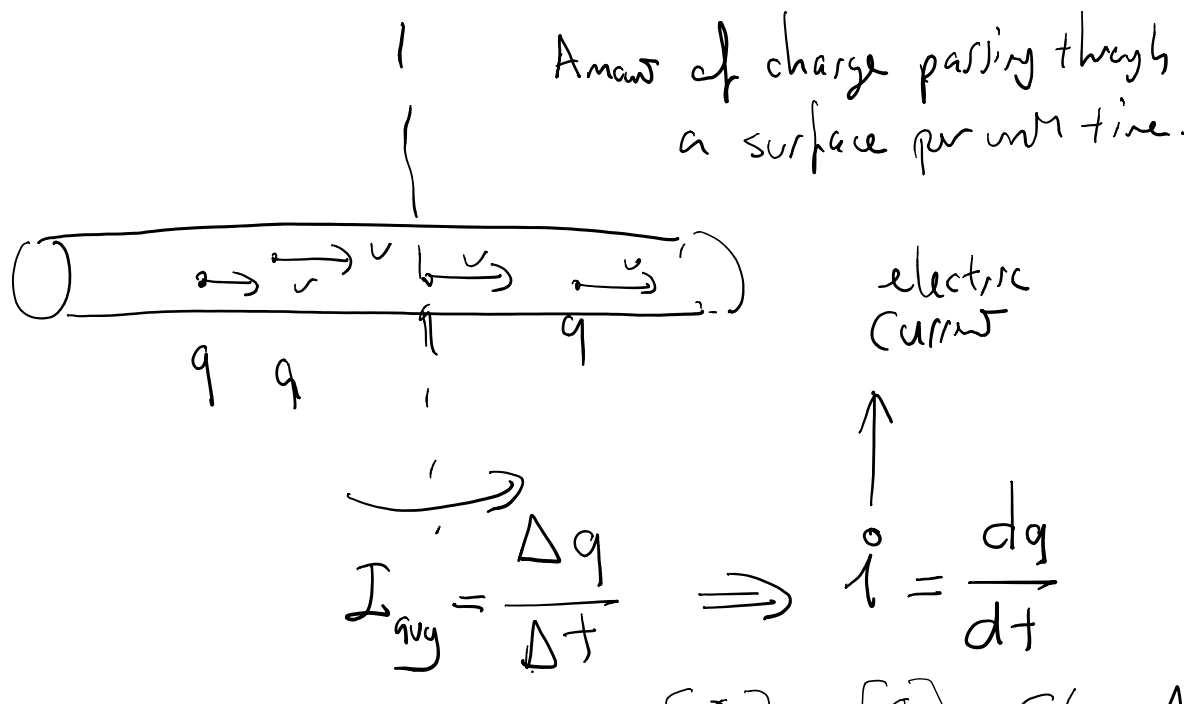


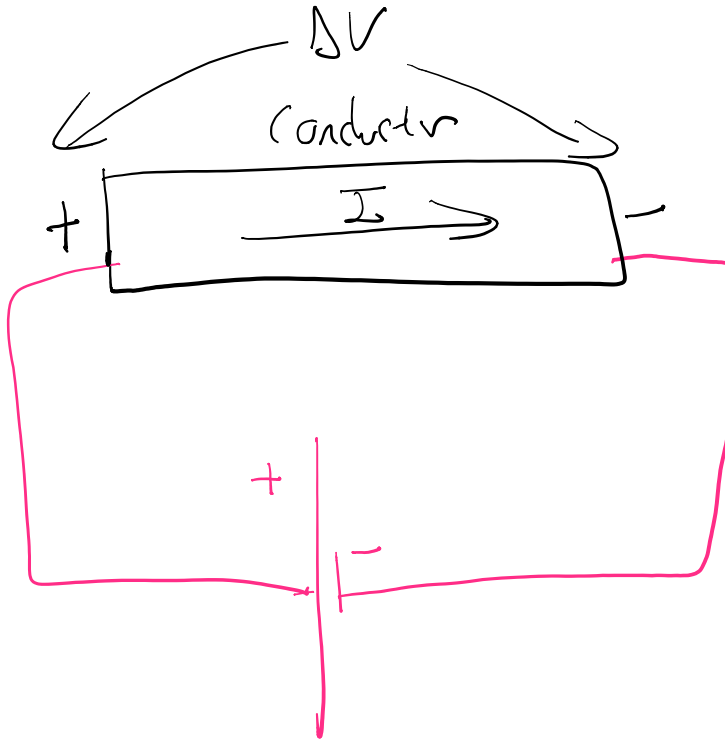
$$[i] = \frac{[q]}{[t]} = \frac{C}{s} = A$$



How does the battery ^{maintain} ~~create~~ this potential difference?

⇒ CHEMISTRY

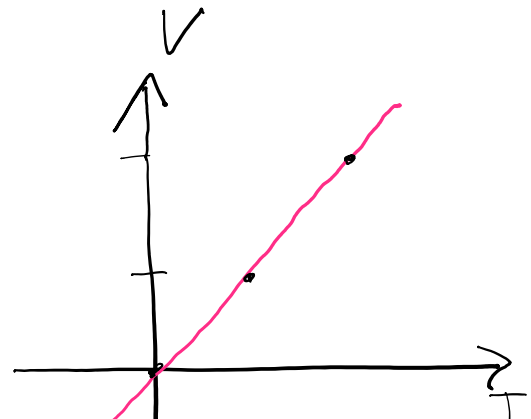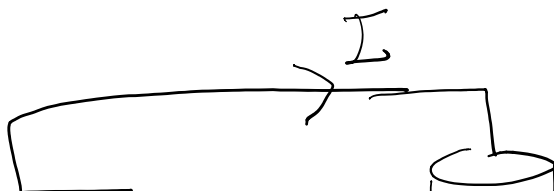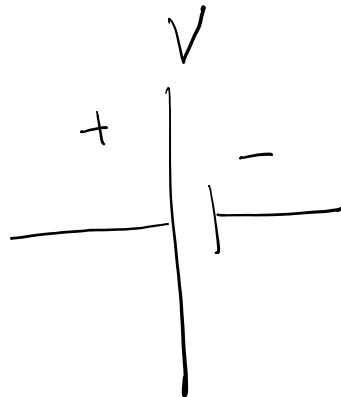


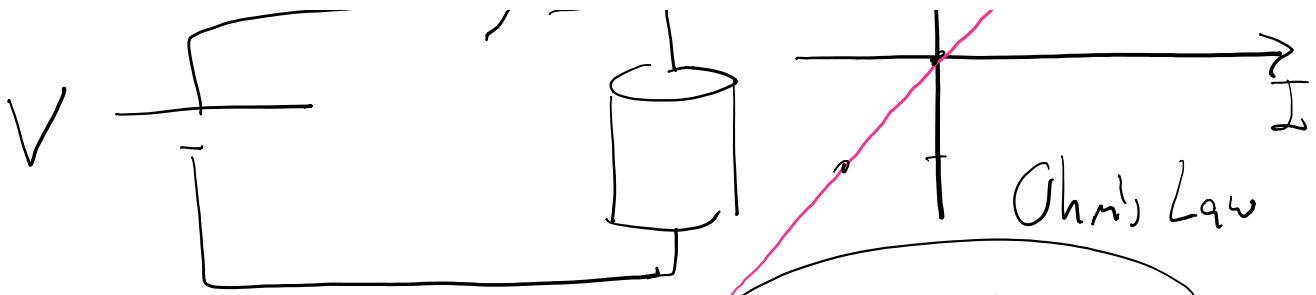

$$V = R I$$

Resistance

Good approximation for most conductors

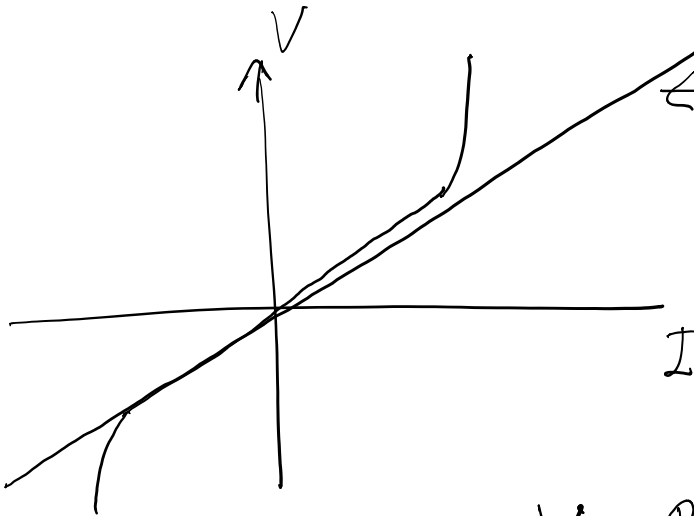

$$V = R I$$

$$[R] = \frac{[V]}{[I]} = \frac{V}{A} = \Omega \text{ "Ohm"}$$

Aside

$$I = G V$$


$$G = \frac{1}{R} \rightarrow \text{conductance}$$

$$[G] = \mathcal{U}$$

"Mho"
Siemens




$$V = R I$$

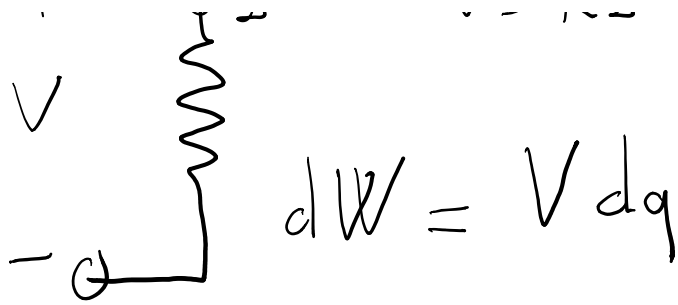

$$\frac{dW}{dt} = \underline{P} = V \frac{dq}{dt} = VI$$

$P = VI \Rightarrow$ energy converted to heat
per unit time across a
resistor.

$$P = I^2 R = \frac{V^2}{R}$$

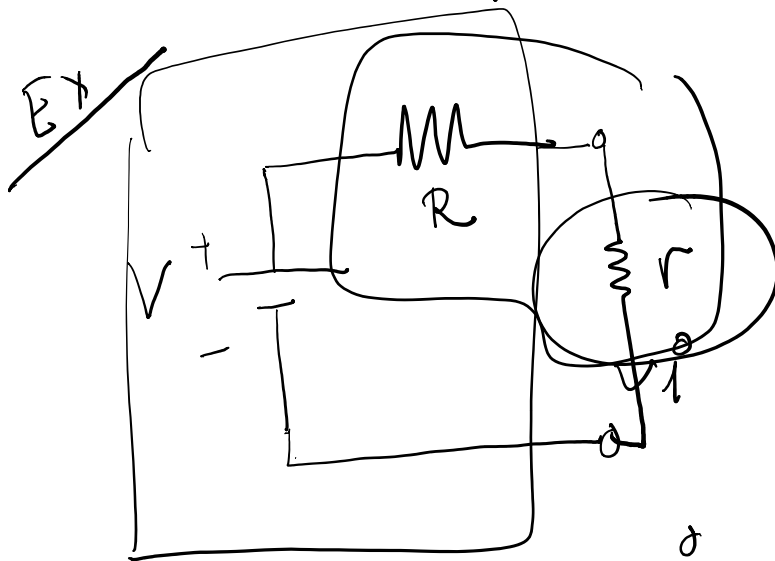

How should we choose r
so that the power
lost on r is maximum.

$$I = \frac{V}{R+r}$$

$$P = I^2 r = \frac{V^2}{(R+r)^2} r$$


$$\frac{\partial P}{\partial r} = \frac{V^2}{(R+r)^2} - \frac{2rV^2}{(R+r)^3} = 0$$

$$\frac{\partial P}{\partial r} = V^2 \frac{(R+r)^2 - r^2 (R+r)}{(R+r)^4} = 0$$

$$R^2 + r^2 + \cancel{2rR} - \cancel{2rR} - 2r^2 = 0$$

$$R^2 = r^2 \Rightarrow \boxed{r = R}$$

Microscopic view of current

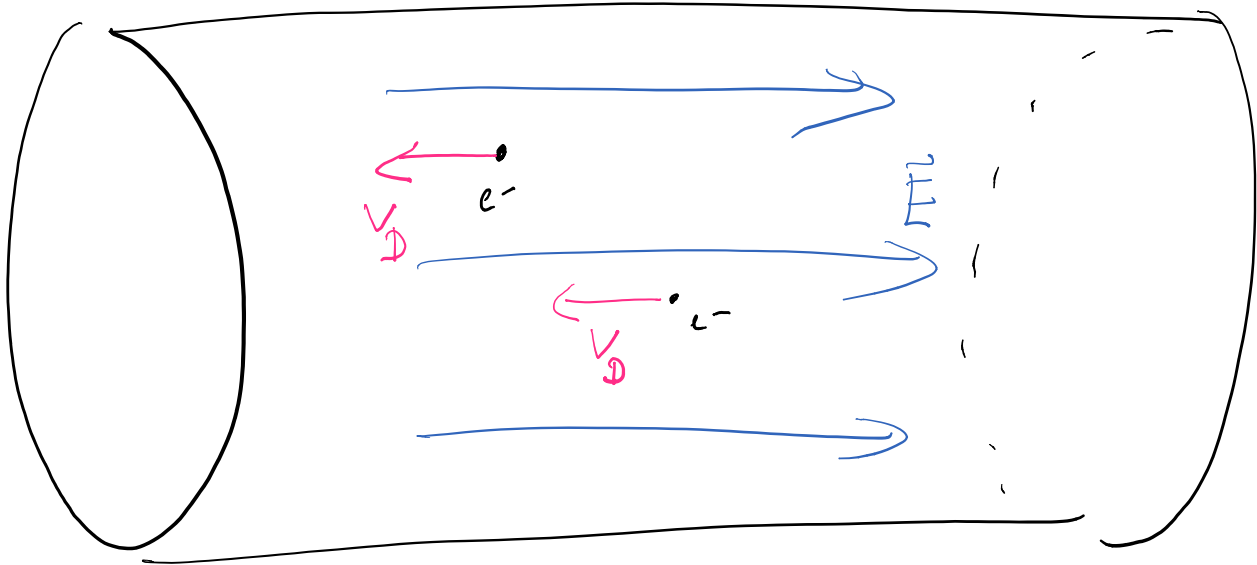


$V_D \rightarrow$ drift velocity

n electrons per unit volume
 each of them have charge $-e$
 all of them move with velocity $\vec{V_D}$


all of them move with velocity v_d
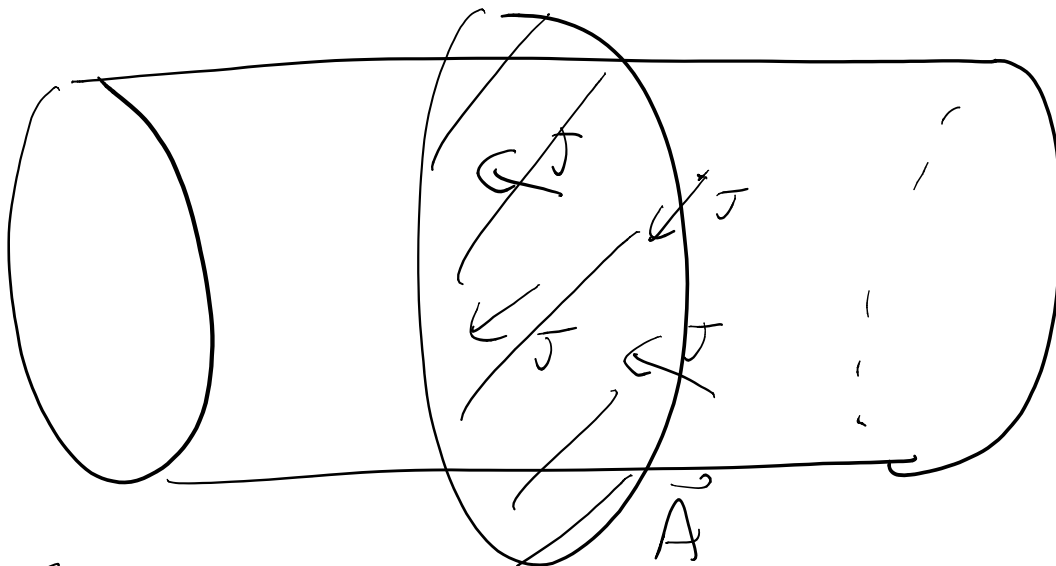
$$\vec{J} = n(-e)\vec{v}_d \Rightarrow \boxed{\text{Current density}}$$



$\int_{\text{cross section}}$

$$\vec{J} \cdot d\vec{A} = I$$

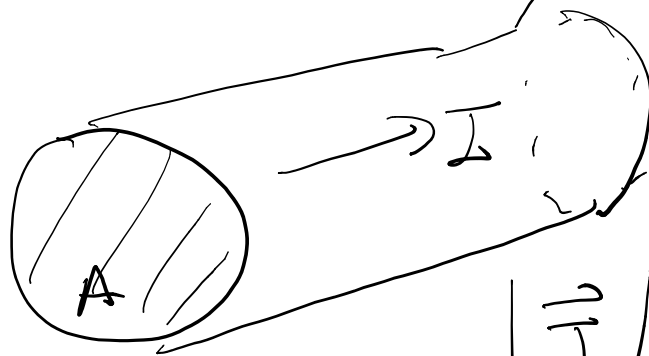

$$|\vec{J}| = \frac{I}{A}$$


$$[\vec{J}] = \text{A/m}^2$$

resistivity

$$\vec{E} = \rho \vec{J}$$

$$\oint \vec{J} = \vec{E}$$

$$\Delta V = \int \vec{E} \cdot d\vec{l} = |\vec{E}| l$$

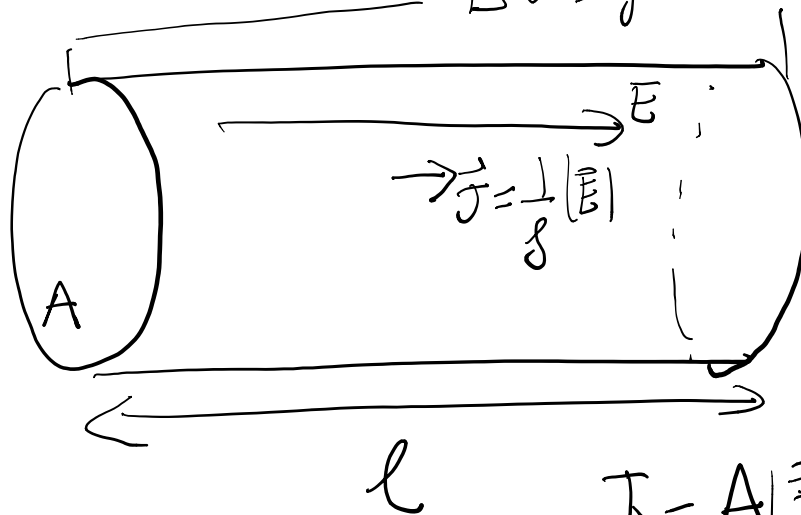

$$I = A |\vec{J}| = \frac{A}{\sigma} |\vec{E}|$$

$$\frac{\Delta V}{I} = \frac{|\vec{E}| l}{\frac{A}{\sigma} |\vec{E}|} = \boxed{\sigma \frac{l}{A} = R}$$

material property


QUIZ-12

An infinite hollow wire is used to carry current. The inside of the wire ($r < a$) is empty, while the region between the inner and outer radii ($a < r < b$) is filled with a material of resistivity ρ .


a) What is the resistance R of a section of the wire that has length L ?

If the wire is carrying a total current of I , which is uniformly distributed,

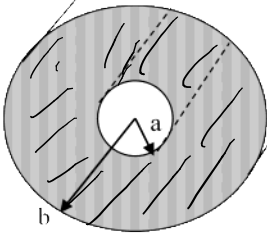b) What is the current density J within the wire?




$$|\vec{J}| = \frac{I}{A} = \frac{I}{\pi(b^2 - a^2)}$$

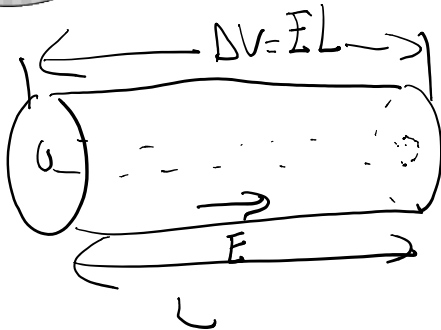

$$|\vec{J}| = \frac{1}{\rho} |\vec{E}|$$

$$I = A \frac{|\vec{E}|}{\rho} = \pi(b^2 - a^2) \frac{|\vec{E}|}{\rho}$$

$$R = \frac{\Delta V}{I} = \frac{|\vec{E}|L}{\pi(b^2 - a^2) \frac{|\vec{E}|}{\rho}} = \boxed{\rho \frac{L}{\pi(b^2 - a^2)}}$$

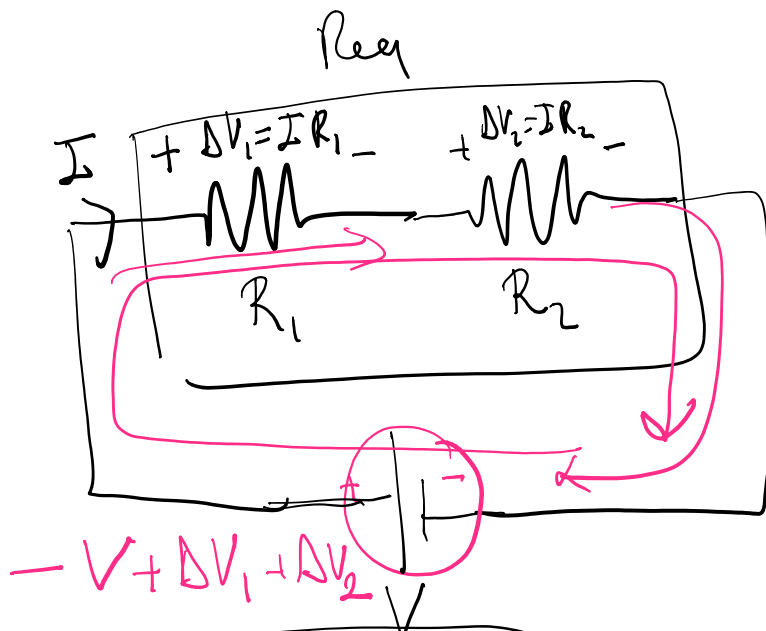


$$V = \Delta V_1 + \Delta V_2$$

$$V = R_1 I + R_2 I$$

$$V = (R_1 + R_2) I$$

$$\boxed{R_{eq} = R_1 + R_2}$$

$$-V + \Delta V_1 + \Delta V_2$$

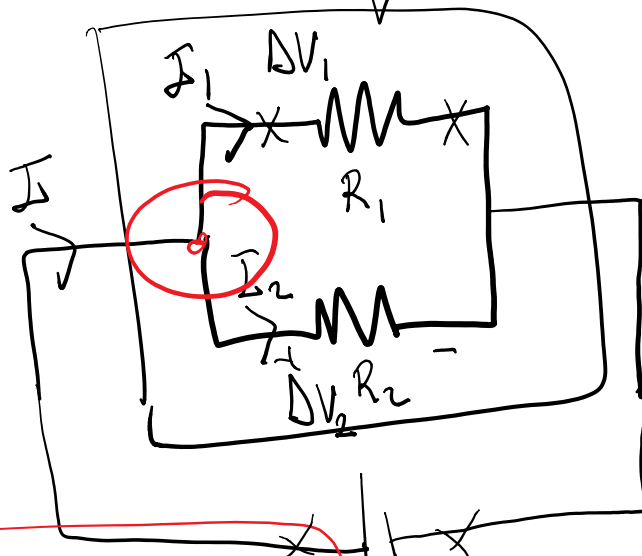

Series

$$\Delta V_1 = V$$

$$I_1 R_1 = V \Rightarrow I_1 = \frac{V}{R_1}$$

$$\Delta V_2 = V$$

$$I_2 R_2 = V \Rightarrow I_2 = \frac{V}{R_2}$$

$$I - I_1 - I_2 = 0$$

$$I = I_1 + I_2$$

$$I = \frac{V}{R_1} + \frac{V}{R_2} = \left(\frac{1}{R_1} + \frac{1}{R_2} \right) V$$

$$V = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} I$$

$$R_{eq}^{-1} = R_1^{-1} + R_2^{-1}$$

All circuits can be solved by the two following principles.


1°) Potential depends only on initial and final points so

$$(\Delta V)_{\text{loop}} = 0$$

2°) At any node

$$\sum (I_{\text{incoming}}) = 0$$

Kirchhoff's Laws

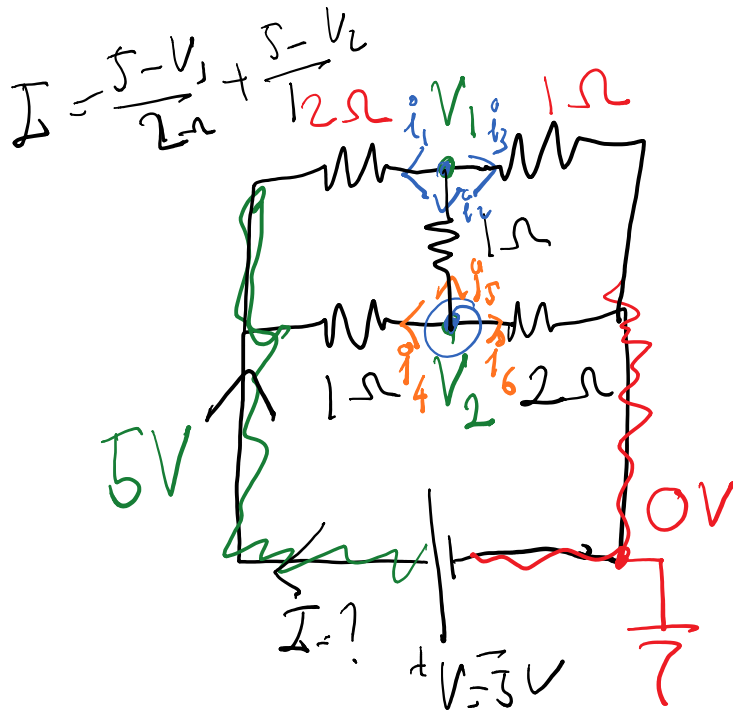

$$i_1 = \frac{V_1 - 5}{2} \quad i_2 = \frac{V_1 - V_2}{1}$$

$$i_3 = \frac{V_1 - 0}{1}$$

$$i_1 + i_2 + i_3 = 0$$

$$\frac{V_1 - 5}{2} + \frac{V_1 - V_2}{1} + \frac{V_1}{1} = 0$$

$$V_1 - 5 + 2V_1 - 2V_2 + 2V_1 = 0$$

$$\boxed{5V_1 - 2V_2 = 5} \quad (1)$$

$$i_4 = \frac{V_2 - 5}{1} \quad i_5 = \frac{V_2 - V_1}{1}$$

$$i_6 = \frac{V_2 - 0}{2}$$

$$i_4 + i_5 + i_6 = 0$$

$$V_2 - 5 + V_2 - V_1 + \frac{V_2}{2} = 0$$

$$2V_2 - 10 + 2V_2 - 2V_1 + V_2 = 0$$

$$5V_2 - 2V_1 = 10 \quad (2^\circ)$$

$$2(5V_1 - 2V_2 = 5)$$

$$5(5V_2 - 2V_1 = 10)$$

$$10V_1 - 4V_2 = 10$$

$$+ 25V_2 - 10V_1 = 50$$

$$21V_2 = 60$$

$$V_2 = \frac{60}{21} \text{ V}$$

$$V_1 = \frac{5 + 2V_2}{5} = \frac{5 + \frac{120}{21}}{5}$$



$$= 1 + \frac{24}{21} = \frac{45}{21} \text{ V} = V_1$$

$$I = \frac{5 - V_1}{2} + \frac{5 - V_2}{1}$$

$$= \frac{5}{2} - \frac{45}{21} + 5 - \frac{60}{21}$$

$$= \frac{15}{2} - \frac{45 + 120}{42} = \frac{15 \times 21 - 165}{42} = 3.57 \text{ A}$$

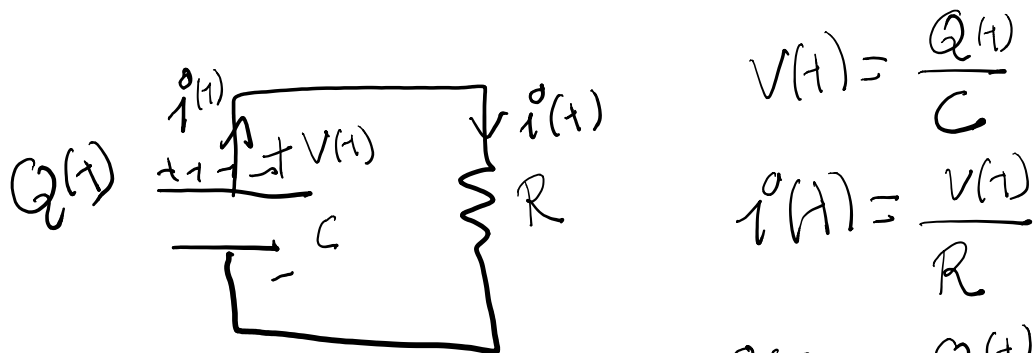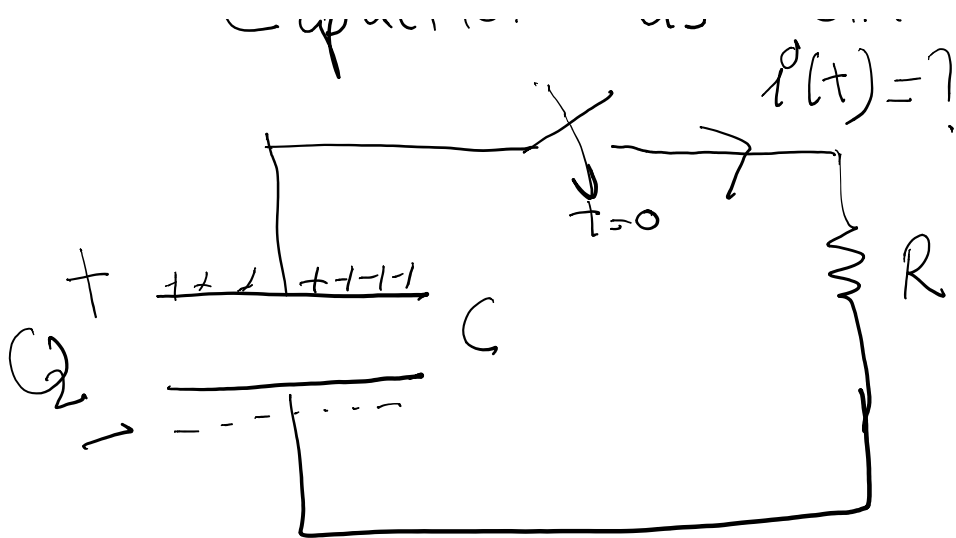Capacitor as circuit element.
 $i(t) = ?$



$$V(t) = \frac{Q(t)}{C}$$

$$i(t) = \frac{V(t)}{R}$$

$$i(t) = \frac{Q(t)}{RC}$$

$$i(t) = -\frac{dQ(t)}{dt}$$

$$-\frac{dQ(t)}{dt} = \frac{Q(t)}{RC}$$

$$\frac{dQ(t)}{dt} = -\frac{1}{RC} Q(t)$$

By inspection

$$Q(t) = A e^{\alpha t}$$


$$\frac{dQ(t)}{dt} = \alpha A e^{\alpha t}$$

$\frac{dQ}{dt}$

$$\propto A e^{\alpha t} = -\frac{1}{RC} A e^{\alpha t} \Rightarrow \boxed{\alpha = -\frac{1}{RC}}$$

$$Q(t=0) = Q = A \underbrace{e^{-\frac{1}{RC} \cdot 0}}_1 \Rightarrow A = Q$$

$$Q(t) = Q e^{-t/RC} \quad e = 2.71828$$

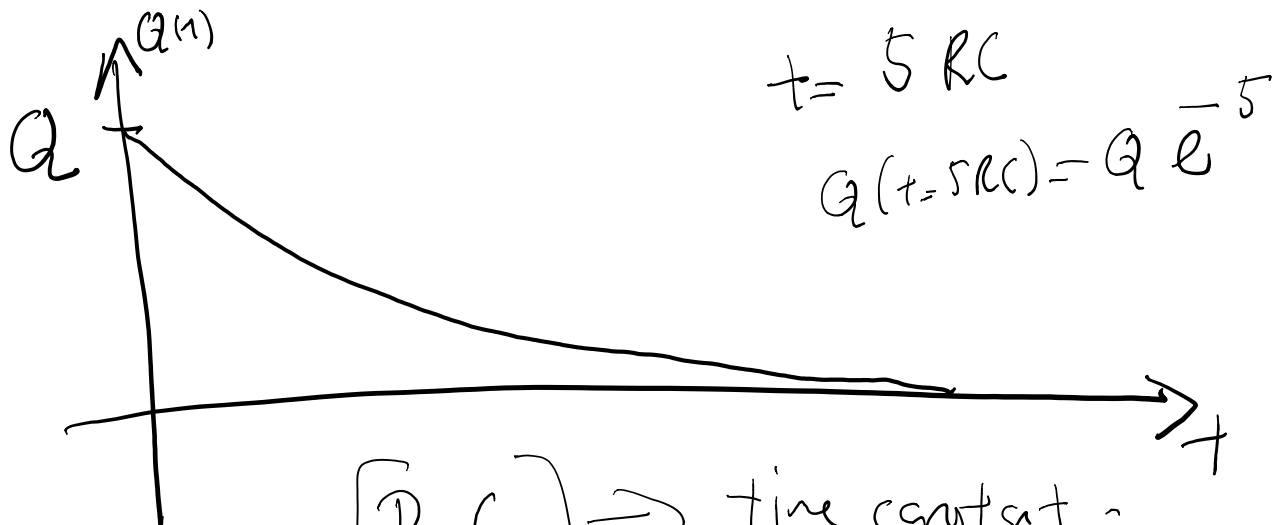

$[RC] \Rightarrow$ time constant "

$$\tau = RC \quad [\tau] = \Omega F = \text{sec}$$

$$Q(t) = Q_0 e^{-t/RC}$$

↓


$$1.6 \cdot 10^{-19} = 1 \cdot e^{-t/1}$$

QUIZ-13
QUIZ-13


A capacitor $C=1 \text{ F}$ is charged with initial charge 1 Coulomb. This capacitor is discharged over a resistor $R=1 \Omega$. How long does it take for the charge of the capacitor to decrease to only a single electron. (Electron

A capacitor $C=1\text{ F}$ is charged with initial charge 1 Coulomb . This capacitor is discharged over a resistor $R=1\ \Omega$. How long does it take for the charge of the capacitor to decrease to only a single electron. (Electron charge is $e = 1.60 \cdot 10^{-19}\text{ C}$.)


$$1.6 \cdot 10^{-19} = 1 e^{-1/1}$$

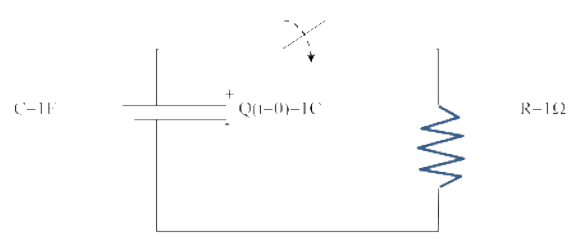
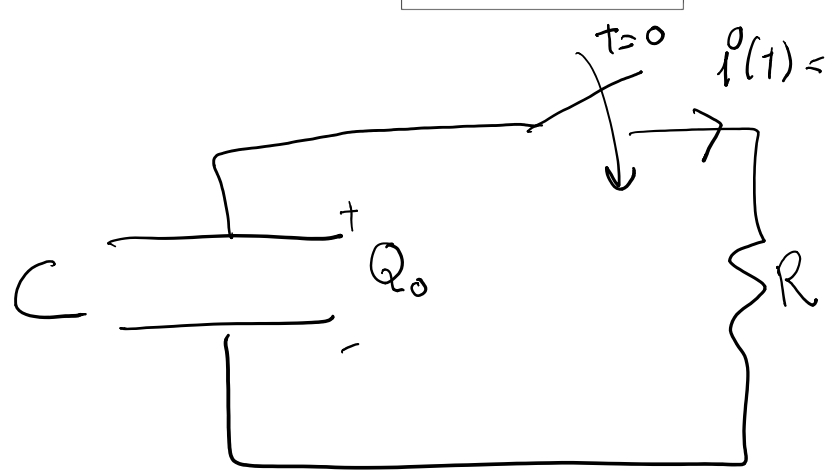
$$t = -\ln(1.6 \cdot 10^{-19}) \text{ sec}$$
$$t = 43.2 \text{ sec}$$



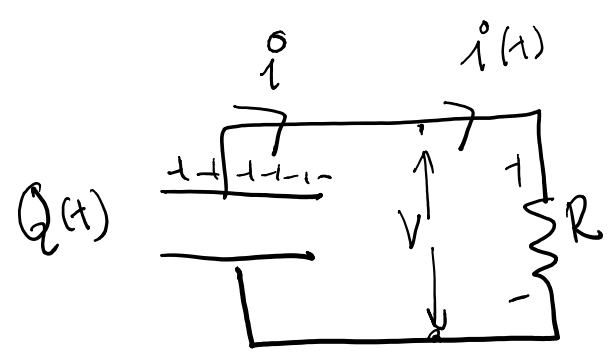$i(t) = ?$ $Q(t) = ?$
Total power dissipated on the resistor.



$$V = \frac{Q(t)}{C} = i(t)R$$

$$\frac{1}{RC} Q(t) = i(t)$$

$$\frac{dQ}{dt} = -i$$

$$\frac{1}{RC} Q(t) = -\frac{d}{dt} Q(t)$$

$$\frac{1}{RC} Q = -\frac{dQ}{dt}$$

$$Q(t) = A e^{\alpha t}$$
$$\frac{dQ}{dt} = \alpha A e^{\alpha t}$$

$$\int_0^T \frac{1}{RC} dt = - \int_{Q_i}^{Q_f} \frac{dQ}{Q}$$

$$\frac{1}{RC} T = - \ln \frac{Q_f}{Q_i}$$

$$Q_f = Q_i e^{-T/RC}$$

$$\frac{1}{RC} A e^{\alpha t} = -\alpha A e^{\alpha t}$$

$$\alpha = -1/RC$$

$$Q(t) = A e^{-t/RC}$$


$$t=0 \quad Q(t=0) = Q_0$$

$$A e^{-0/RC} = Q_0$$

$$Q(t) = Q_0 e^{-t/RC}$$

$$\tau = RC$$



time constant

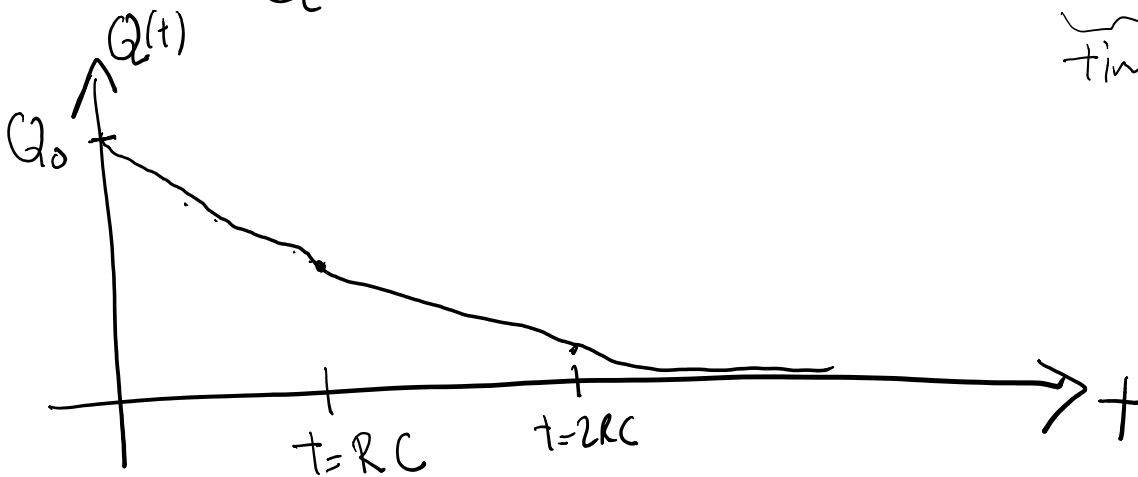


$$Q(t=\tau) = Q_0 e^{-1}$$

$$Q(t=2\tau) = Q_0 e^{-2}$$

Charging a capacitor

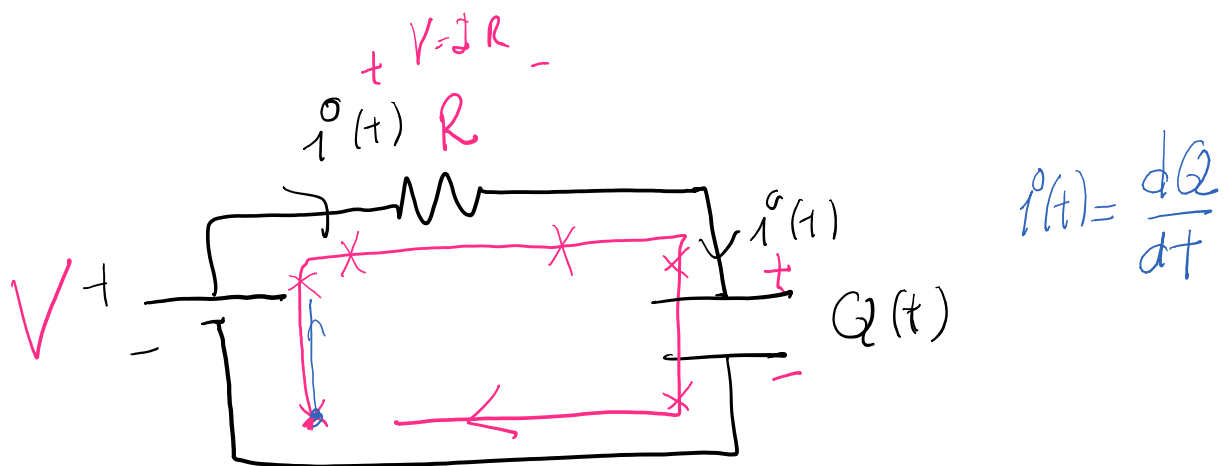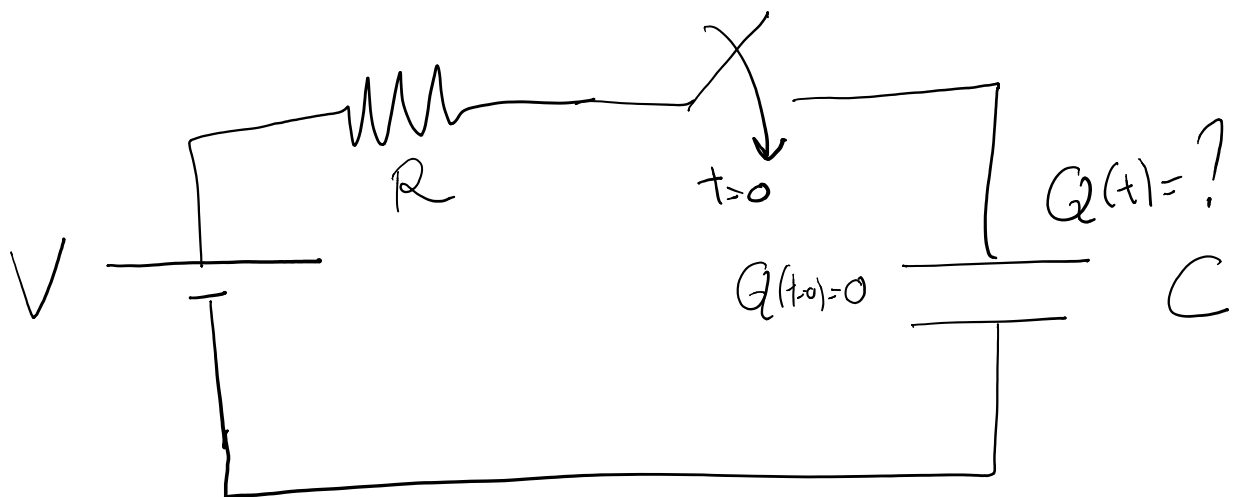

$$V - i(t)R - \frac{Q(t)}{C} = 0$$

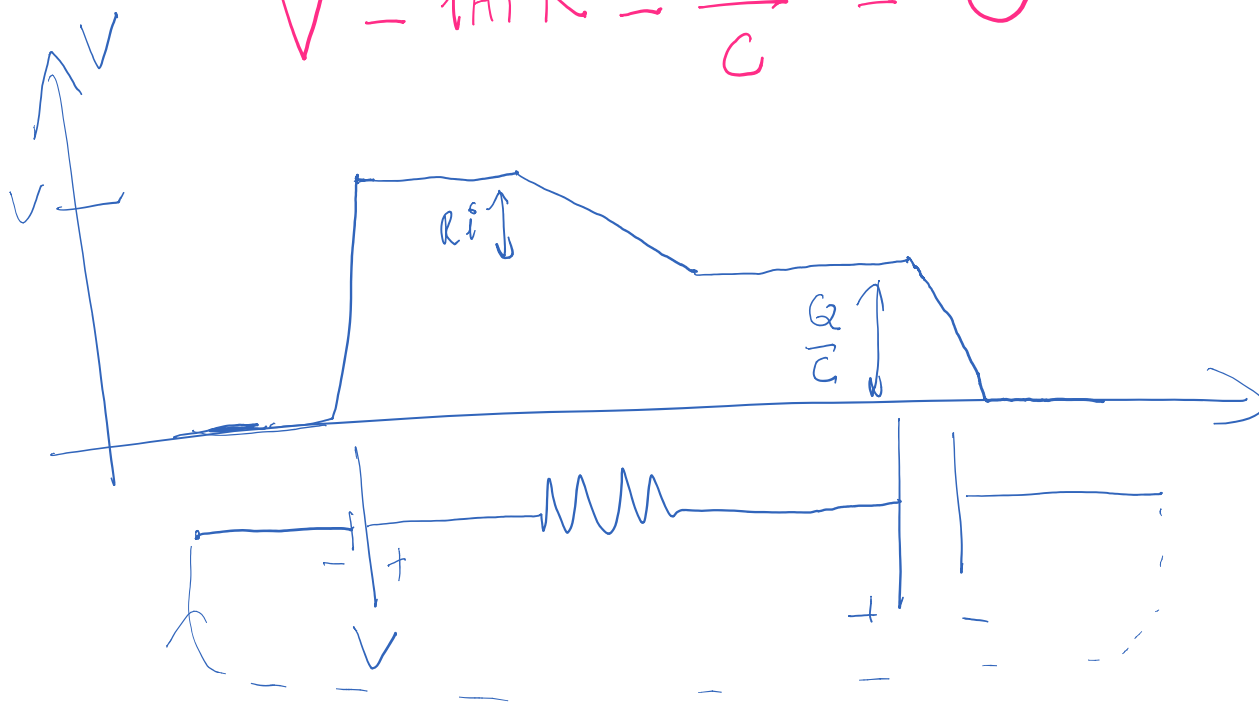

$$V - i(t)R - \frac{Q(t)}{C} = 0$$

$$V - R \frac{dQ(t)}{dt} - \frac{1}{C} Q(t) = 0$$

$$\frac{dQ(t)}{dt} = \left(\frac{V}{R} - \frac{1}{RC} Q(t) \right)$$

Define $q(t) = VC - Q(t) \Rightarrow Q(t) = VC - q(t)$

$$\boxed{\frac{dq}{dt} = - \frac{dQ}{dt}}$$

$$- \frac{dq}{dt} = \frac{1}{RC} \underbrace{(VC - Q(t))}_{q(t)}$$

$$\boxed{\frac{dq}{dt} = - \frac{1}{RC} q(t)}$$

$$q(t) = q_0 e^{-t/RC}$$


$$Q(t=0) = 0$$

$$q_0 = VC - Q(t=0) = VC$$


$$q(t) = VC e^{-t/RC}$$

$$Q(t) = VC - VC e^{-t/RC}$$

$$Q(t) = VC (1 - e^{-t/RC})$$

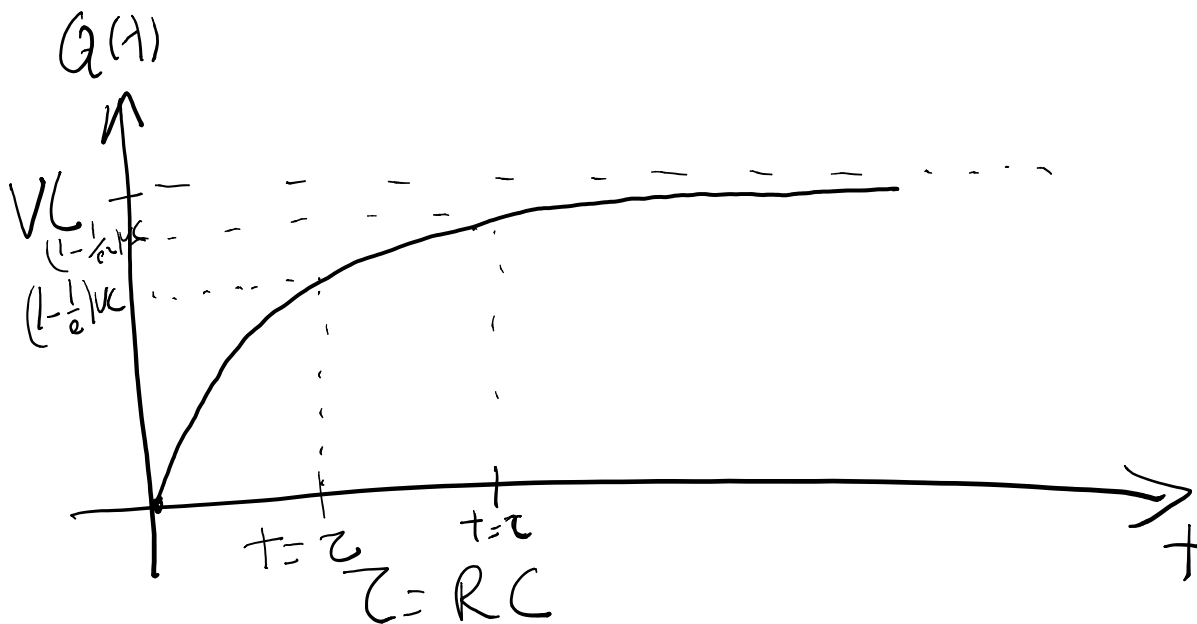

EX

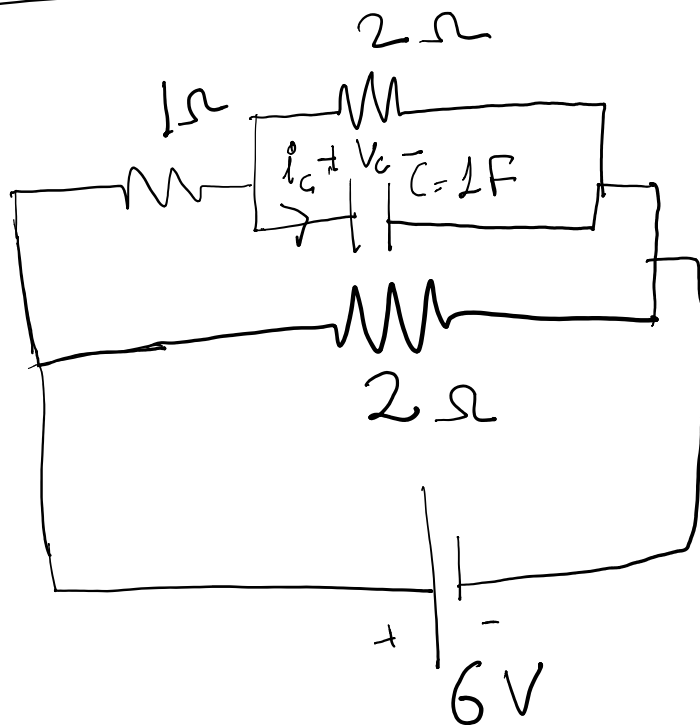


If we wait for very long time so that the system is in steady state what is the charge on the capacitor.

$$\frac{dV}{dt} \rightarrow 0 \quad \frac{dI}{dt} \rightarrow 0$$

Steady state $\frac{dV}{dt} \rightarrow 0$ $\frac{dI}{dt} \rightarrow 0$
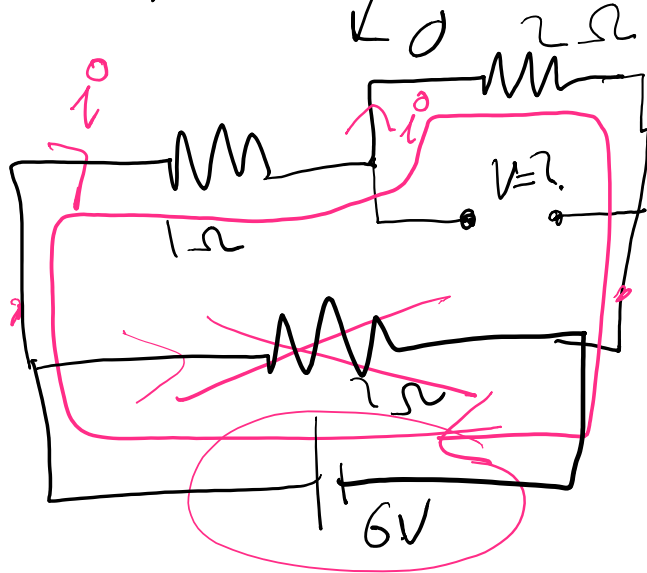
$$i_c = \frac{dQ}{dt} = C \frac{dV}{dt} \xrightarrow{\text{steady state}} i_c = 0$$



$$6V = i1\Omega + i2\Omega$$

$$6 = 3i$$

$$i = 2A$$

$$V = i2 = \boxed{4V}$$

$$Q = CV = \boxed{4C}$$